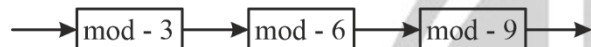


1. If Mod-60 counter is cascaded with Mod - 40 counter, then it will becomes,

(a) Mod - 100 counter
(b) Mod - 2400 counter
(c) Mod - 20 counter
(d) Mod - 140 counter

2. The maximum decimal count of 7-bit asynchronous counter is ____.


3. The modulus of given block is,



(a) 81 (b) 40
(c) 144 (d) 162

4. If input frequency of clock is 10 KHz then output frequency of counter will be ____ KHz [Assume mod of counter is 5]

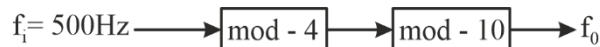5. For given block, the value of f_0 is ____ Hz.



6. Symmetric square wave of time period 100 μ sec can be obtained from square wave of time period 10 μ sec by using a

(a) divide by - 5 circuit
(b) divide by - 2 circuit
(c) divide by - 5 followed by a divide by 2 - circuit
(d) None of these

7. How many flip - flops are required to construct Mod-31 counter?

(a) 4 (b) 3
(c) 2 (d) 5

Answer Key

1. (b)
2. (127)
3. (d)
4. (2)

5. (12.5)
6. (c)
7. (d)



Any issue with DPP, please report by clicking here:- <https://forms.gle/t2SzQVvQcs638c4r5>

For more questions, kindly visit the library section: Link for web: <https://smart.link/sdfez8ejd80if>



PW Mobile APP: <https://smart.link/7wwosivoicgd4>