

CS & IT ENGINEERING



DIGITAL LOGIC Sequential Circuit



Lecture No. 11



By- CHANDAN SIR

Recap of Previous Lecture



Sequential Circuit

Asynchronous Counter-

Topics to be Covered




Sequential Circuit

▪ **Questions Practice**

(MCQ)


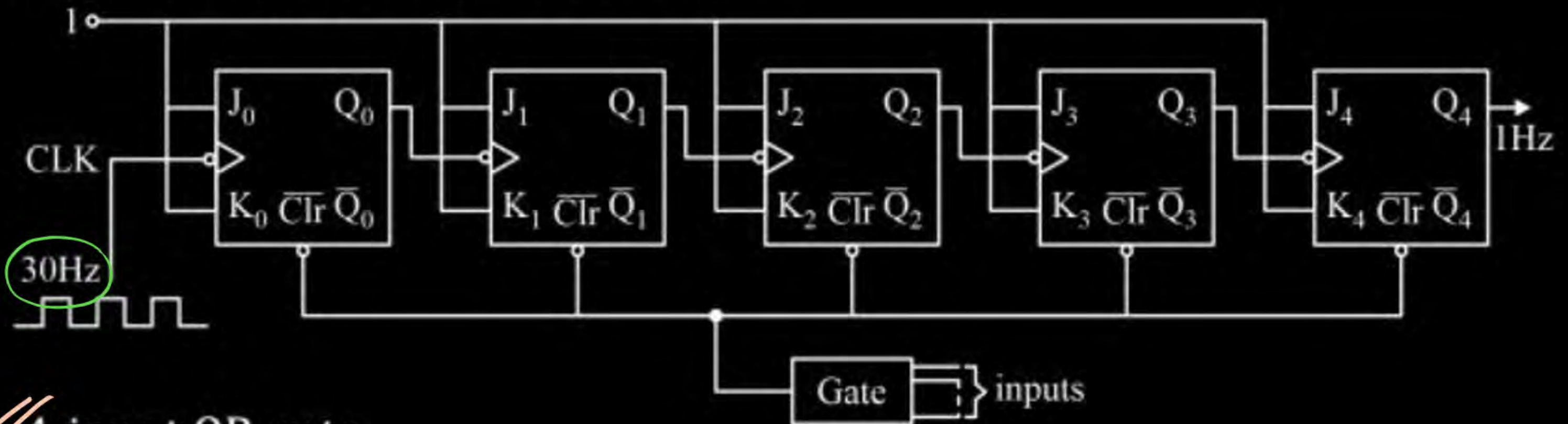
#Q. Consider the following counter as shown below is needed to divide the 30 Hz line frequency down to 1 Hz. \bar{Q} output is used in input of gate. Required logic gate for this counter is,




- ☒ **A** 4-input OR-gate
- ☐ **B** 3-input NAND-gate
- ☐ **C** 4-input NAND-gate
- ☐ **D** 4-input NOR-gate

$$f_{out} = \frac{f_{in}}{M}$$
  
$$M = \frac{f_{in}}{f_{out}} = \frac{30\text{Hz}}{1\text{Hz}} = 30$$




NOR → for active high

 

for active low


(MCQ)
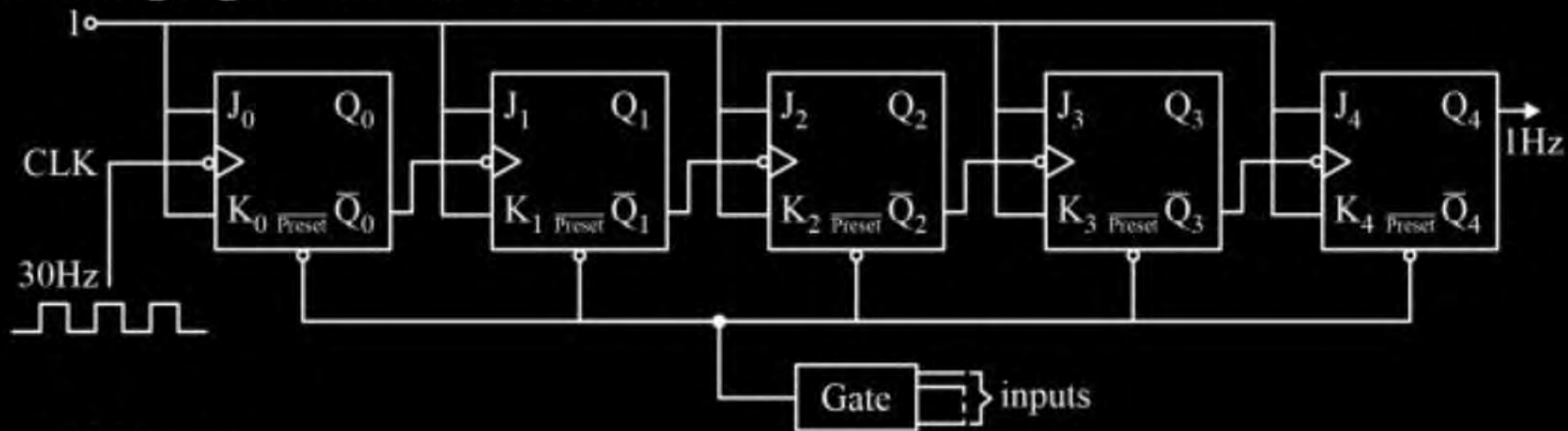
#Q. Consider the following counter as shown below is needed to divide the 30 Hz line frequency down to 1 Hz. Q output is used in input of gate. Required logic gate for this counter is




- A** 3-input OR-gate
- B** 3-input NOR-gate
- C** 4input NAND-gate
- D** 4-input OR gate

MOD-30 Down Ripple counter

 


Active High


$P_r = 00001$

 

Active Low

 


Active Low

 

Bubbled NAND = OR

(MCQ)
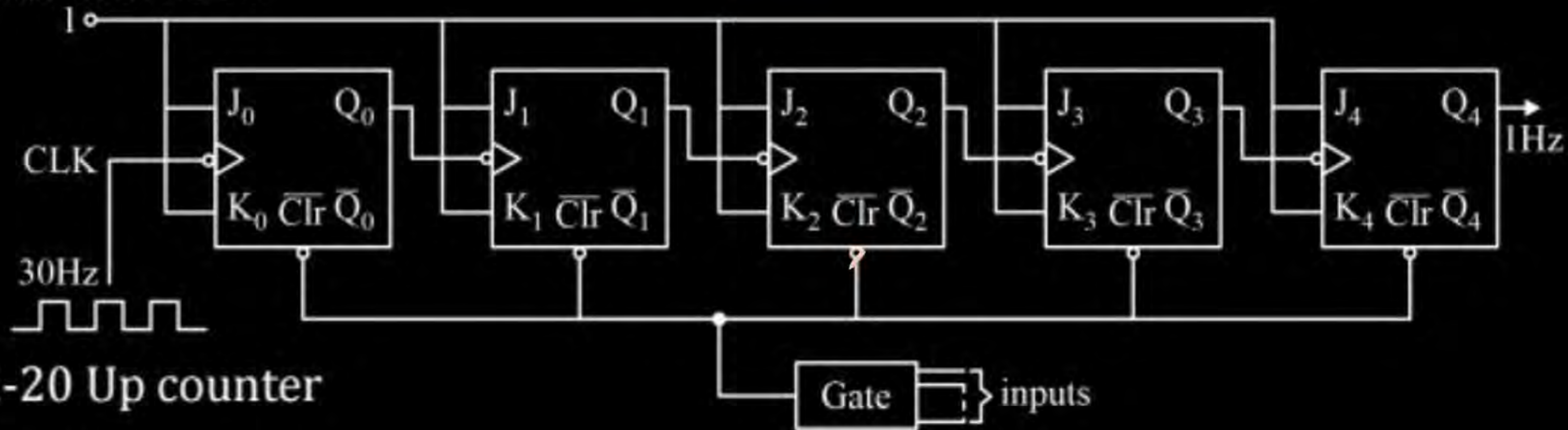
#Q. Counter circuit as shown in figure given below, if all the FFs outputs(Q) are connected as the inputs of the NAND-gate with Q_3 , Q_1 and Q_0 HIGH and rest are LOW. $\overline{\text{Clr}}$ pin is synchronous with clock, then the ripple counter works as



- A** mod-20 Up counter
- B** mod-11 Up counter
- C** mod-11 Down counter
- D** mod-12 Up counter

$$clr = \overline{Q_4} Q_3 \overline{Q_2} Q_1 Q_0$$

$$= 0 \ 1 \ 0 \ 1 \ 1 \rightarrow 11$$

Asynchronous clear

0 → 10

MOD-11 UP

→ state at which Reset/Preset occurs don't count.


Synchronous Reset/Preset

→ state at which Reset/Preset occurs we have to count.

0 → 11 → MOD-12 UP

(MCQ)
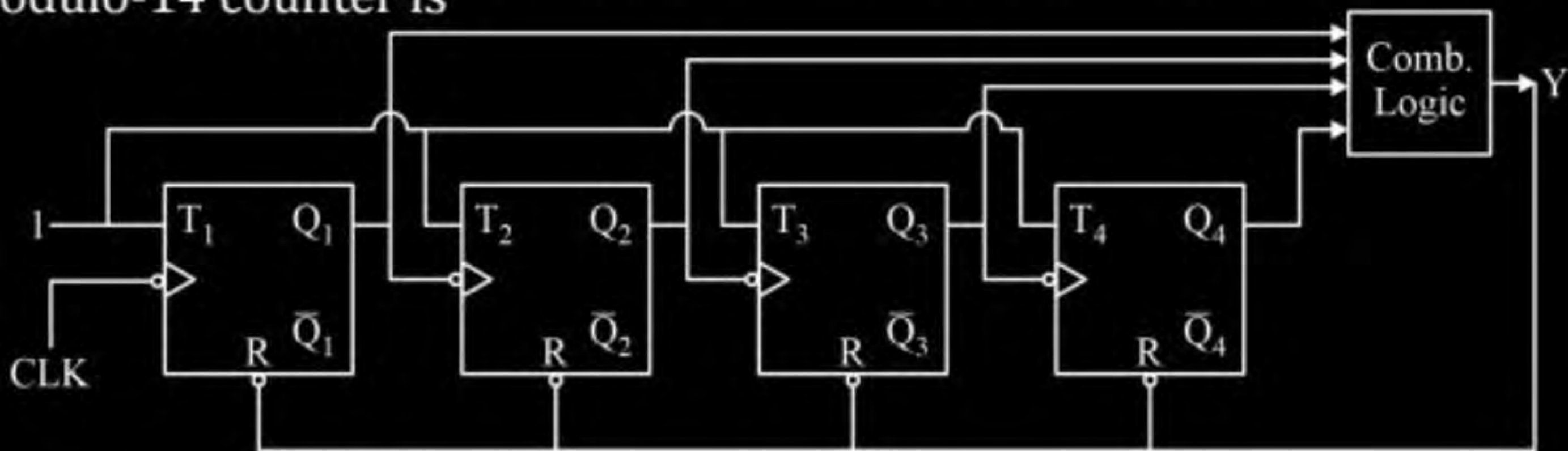
#Q. The counter shown in figure is built with 4-toggled FFs. The FFs can be set asynchronous clear when $R = 0$. The logic required to realize a modulo-14 counter is




- A** $Y = \bar{Q}_4 + \bar{Q}_3 + \bar{Q}_2 + Q_1$
- B** $Y = Q_4 Q_3 Q_2 \bar{Q}_1$
- C** $Y = Q_4 + Q_3 + Q_2 + \bar{Q}_1$
- D** $Y = \bar{Q}_4 \bar{Q}_3 \bar{Q}_2 Q_1$

MOD-14 UP

clr = 1 1 1 0



Active high

 


$$R = \overline{Q_3 \cdot Q_2 \cdot Q_1 \cdot Q_0}$$

$$= \overline{Q_3} + \overline{Q_2} + \overline{Q_1} + \overline{Q_0}$$

(NAT)
 
#Q. Consider an asynchronous counter design as shown below.

Assume Q_0 is the output of LSB FFs and Q_5 is the output of MSB FF and all J, K inputs are logically at '1'. $\overline{\text{Clr}}$ pin is synchronous, the mod number 'N' for this given counter is _____.



$$Clr = Q_5 \bar{Q}_4 Q_3 Q_2 \bar{Q}_1 Q_0$$

$$1 \ 0 \ 1 \ 1 \ 0 \ 1 \longrightarrow (45)$$

Asynchronous Reset

0 — 44

MOD = 95 UP

synchronous Reset


0 — 45

MOD = 46 UP

(MCQ)
 
#Q. Assuming all $J = K = 1$ in the counter shown below, find the counting sequence

- A** 000 to 111
- B** 111 to 000
- C** 100 to 000
- D** 000 to 110



UP counter


Clr = (111) X

000 → 110
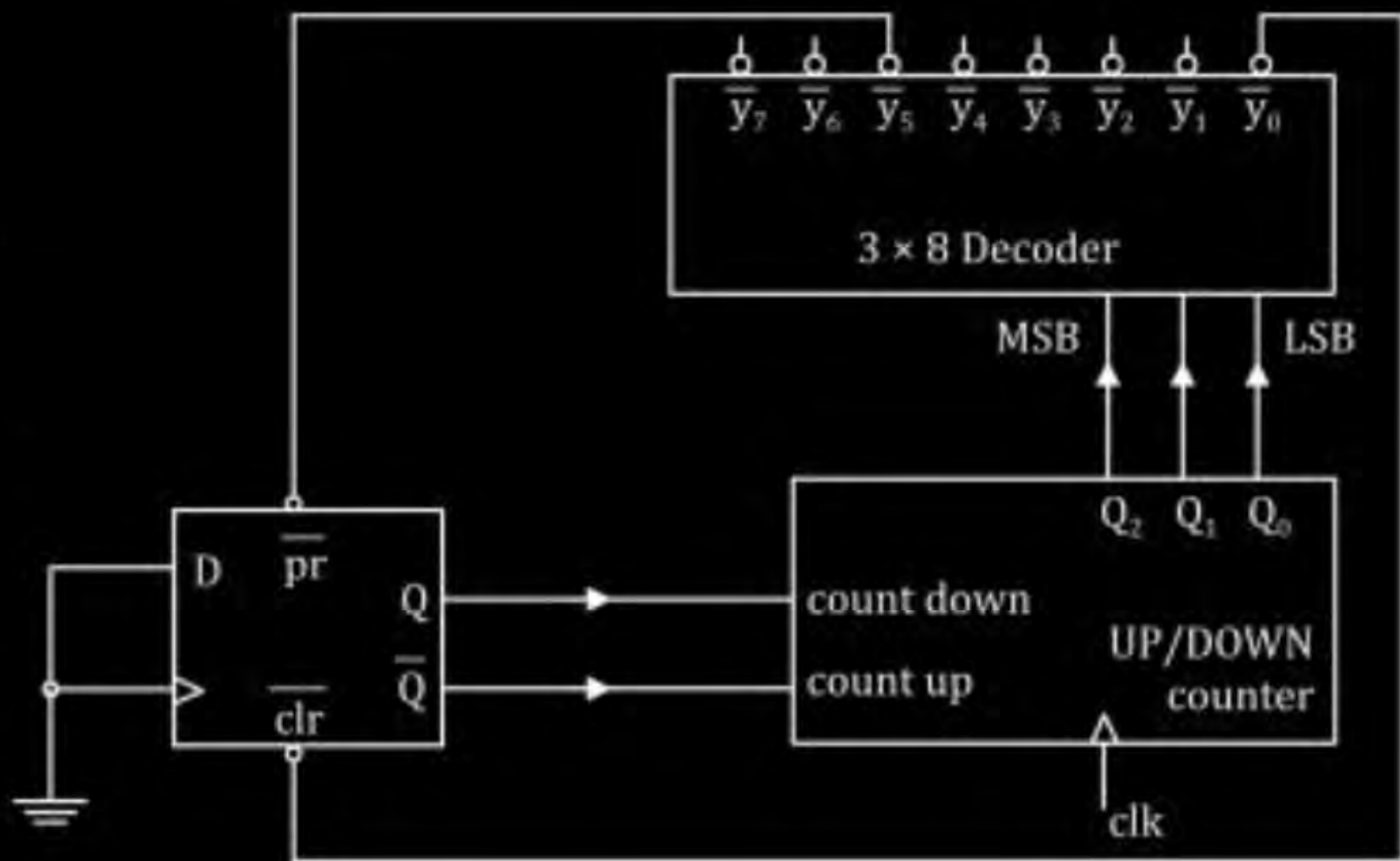
#Q.

A flip flop with active low preset and clear, a 3×8 decoder and a up/down counter, are interconnected as shown below. Assume initially $Q_2 = Q_1 = Q_0 = 0$. The counter outputs in decimal for 12 clock pulses, will be

- A** 0, 1, 2, 3, 4, 4, 3, 2, 1, 1, 2, 3, 4
- B** 0, 1, 2, 3, 4, 5, 0, 1, 2, 3, 4, 5, 0
- C** 0, 1, 2, 3, 4, 5, 5, 4, 3, 2, 1, 0, 1
- D** 0, 1, 2, 3, 4, 5, 4, 3, 2, 1, 0, 1, 2




	Q_2	Q_1	Q_0
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	0	0
7	0	1	1
8	0	1	0
9	0	0	1
10	0	0	0
11	0	0	1
12			

$0 \rightarrow 1 \rightarrow 2 \rightarrow 3 \rightarrow 4 \rightarrow 5 \rightarrow 4 \rightarrow 3 \rightarrow 2 \rightarrow 1 \rightarrow 0$
 \downarrow
 $3 \leftarrow 2 \leftarrow 1$
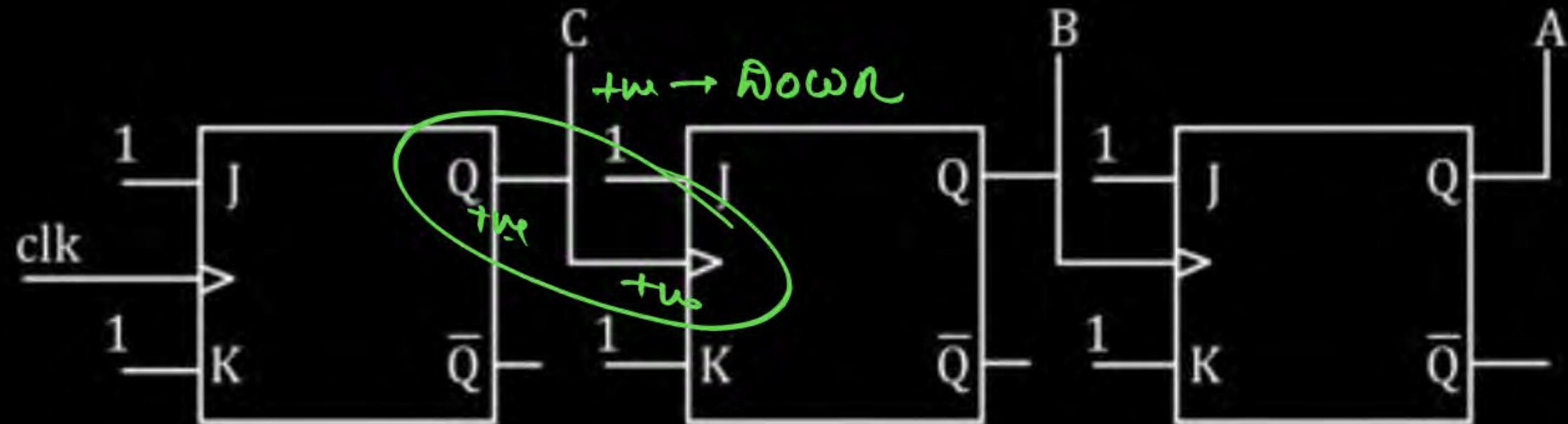
#Q.

The circuit shown below, is a 3-bit ripple counter with A as MSB. The flip flops in the circuit, are rising edge triggered. The counting direction is



- A** always up
- B** ✓ always down
- C** up or down depending on initial state of C
- D** up or down depending on initial state of C, B and A.


#Q.



A circuit for truncated ripple counter together with a reset function labelled y , is shown below

The reset function y can be expressed as

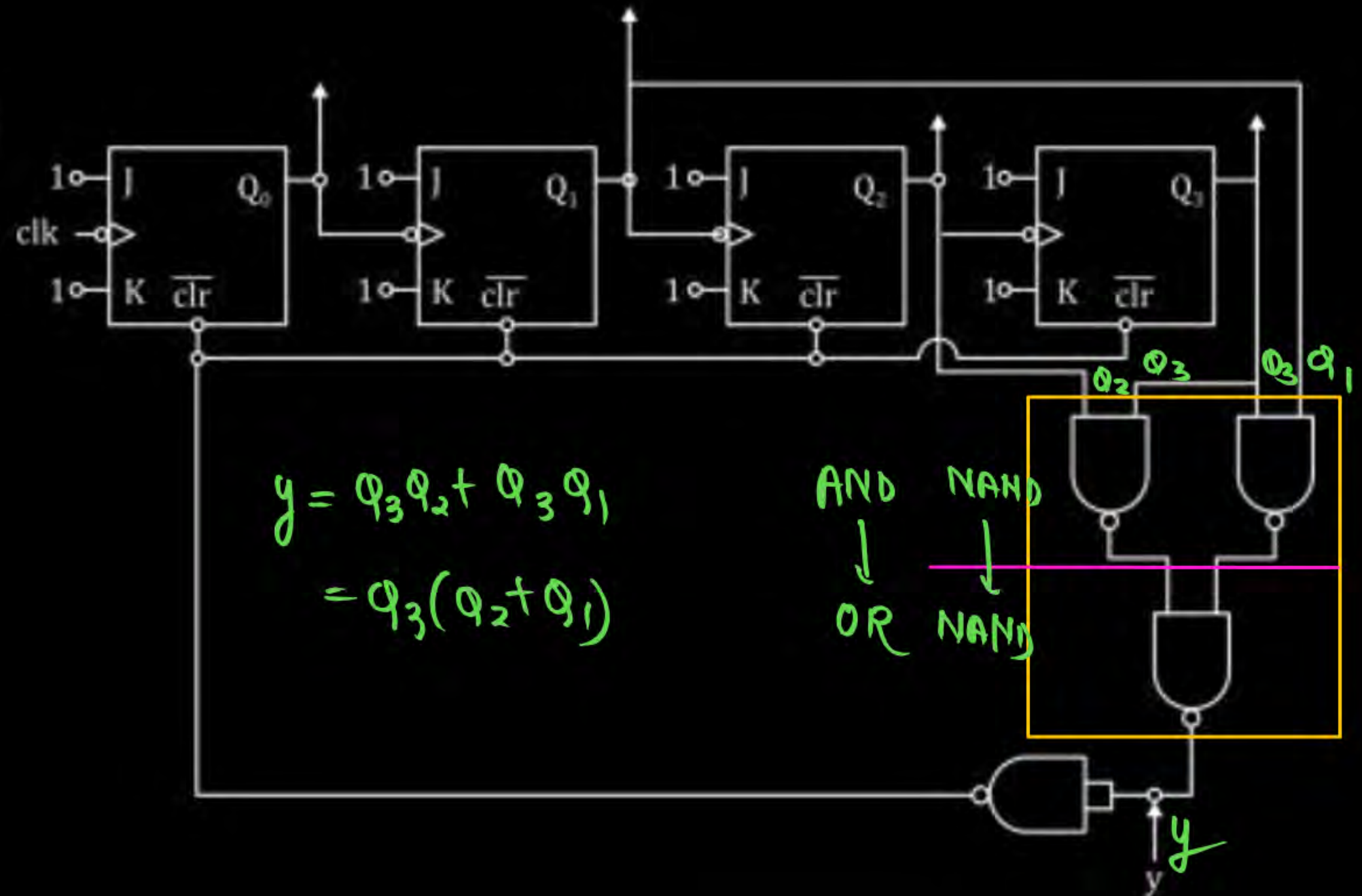
- A** ✓ $y = Q_3 (Q_2 + Q_1)$
- B** $y = Q_3 + Q_2 Q_1$
- C** $y = \overline{Q_3 (Q_2 + Q_1)}$
- D** $y = \overline{Q_3 + Q_2 Q_1}$



#Q.

In the figure shown below, initially $ABC = 000$. After three clock pulses, the state ABC will be


- A** 110
- B** 011
- C** 001
- D** 101

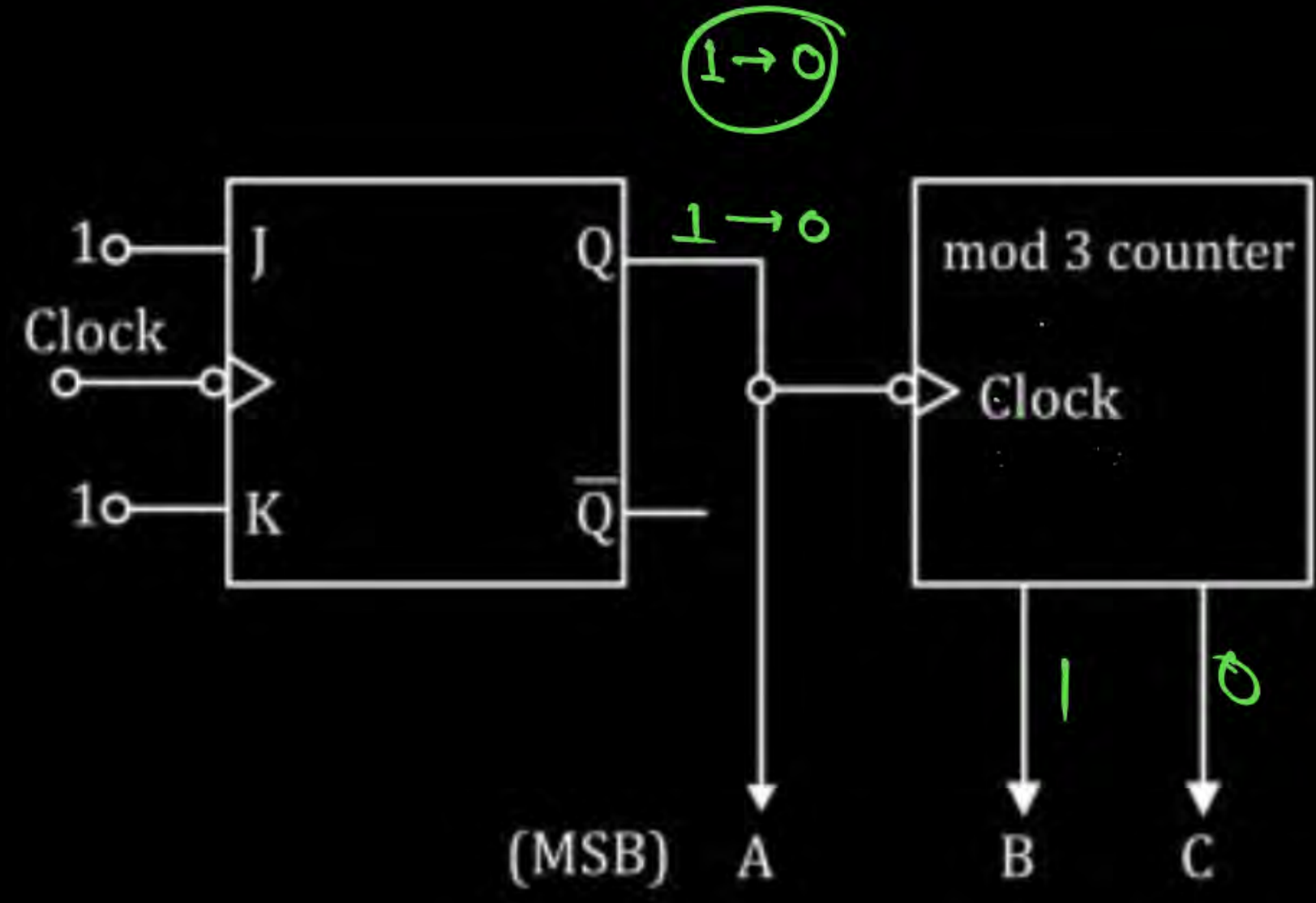

Clock	A	B	C
0	0	0	0
1	1	0	0
2	0	0	1
3	1	0	1
4	0	1	0

A sequential circuit is as given below has total 20 FFs connected. If input clock frequency is 128 MHz, at output of 16th FF frequency of the waveform will be:

 - A** 8 MHz
- B** 12.8 MHz
- C** 1.95 KHz.
- D** 4 MHz



$$f_{in} = 128 \text{ MHz}$$

$$f_{Q_{15}} = \frac{f_{in}}{2^{16}} = \frac{128 \times 10^6 \text{ Hz}}{2^{16}} = \frac{128 \times 10^6}{2^{29}} = \frac{1000 \text{ kHz}}{2^9} = \frac{1000 \text{ kHz}}{512}$$

16th FF o/p

NOTE

$$\text{freq} \rightarrow K \rightarrow 10^3 = 1000$$


$$\text{In Binary } K = 2^{10} = 1024 \\ (\text{bit})$$

Question

(MCQ)

A sequential circuit is as given below:
 Both the FFs are at reset state initially, then MOD-no. of the counter is

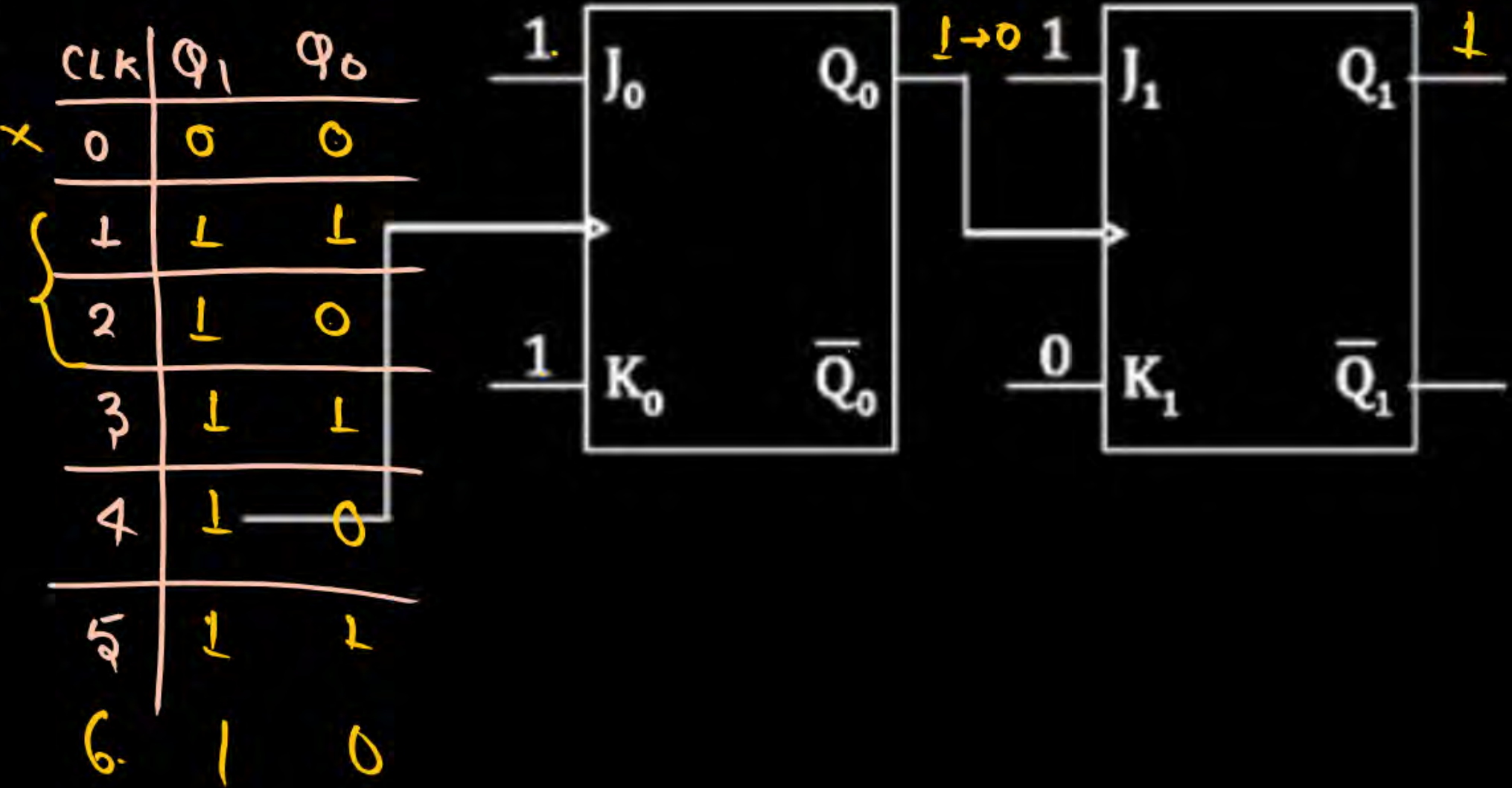- A MOD-4 counter
- B MOD-3 counter
- ☒ C MOD-2 counter
- D None of these





2 Min Summary



Sequential Circuit



Thank You
GW
Soldiers!

