

CS & IT ENGINEERING



DIGITAL LOGIC


Sequential Circuit
Dpp 02 Discussion



By- CHANDAN SIR



TOPICS TO BE COVERED

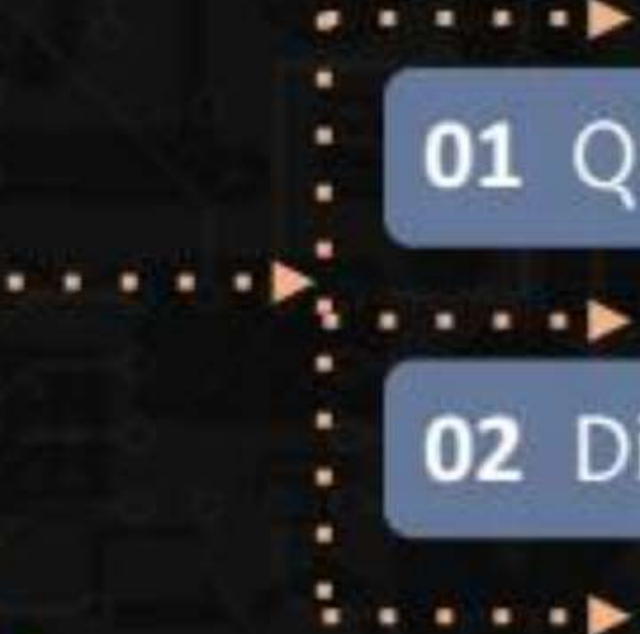

01 Questions

02 Discussion

Q.1

Consider the following J-K flip-flop

In the above J-K flip-flop, $J = \bar{Q}$ and $K = 1$. Assume that the flip-flop was initially cleared and then clocked for 6 pulses. What is the sequence at the Q output?

A.

010000

B.


011001

C.

010010

☒ D.

010101

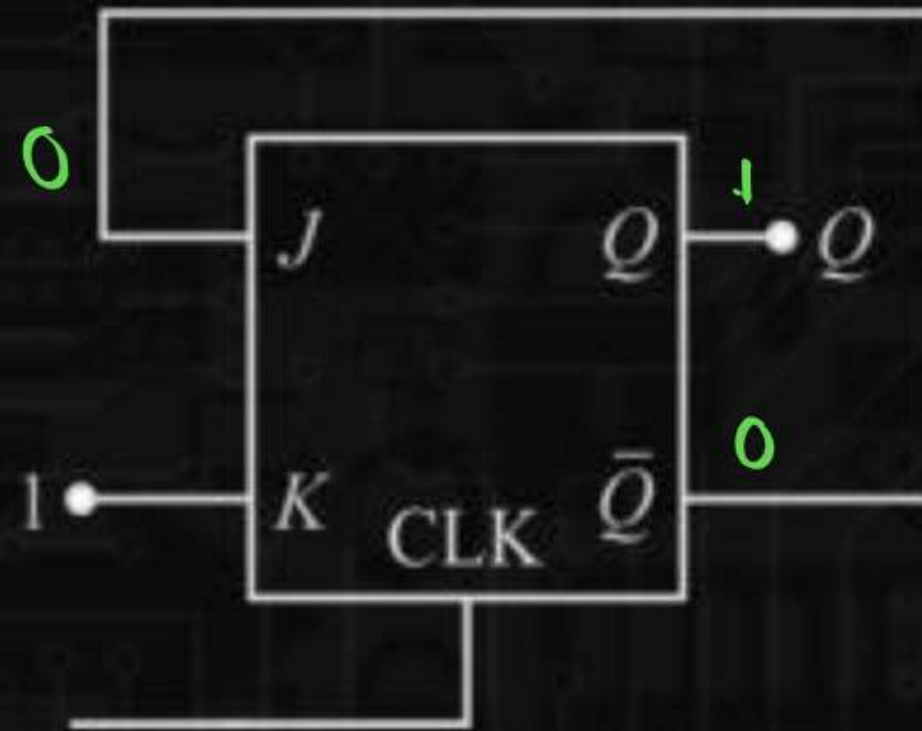

$0 \rightarrow 1 \rightarrow 0 \rightarrow 1 \rightarrow 0 \rightarrow 1 \rightarrow 0$

Q.2

Consider the given circuit.
In this circuit, the race around



SR ✓

A. does not occur.

B. occurs when $CLK = 0$.

C. occurs when $CLK = 1$ and $A = B = 1$.

D. occurs when $CLK = 1$ and $A = B = 0$.


Q.3

A sequential circuit using D Flip-Flop and logic gates is shown in figure, where X and Y are the inputs and Z is the output. The circuit is



$$Q_{n+1} = S + \bar{R}Q_n$$

$$Q_{n+1} = J\bar{Q}_n + \bar{K}Q_n$$

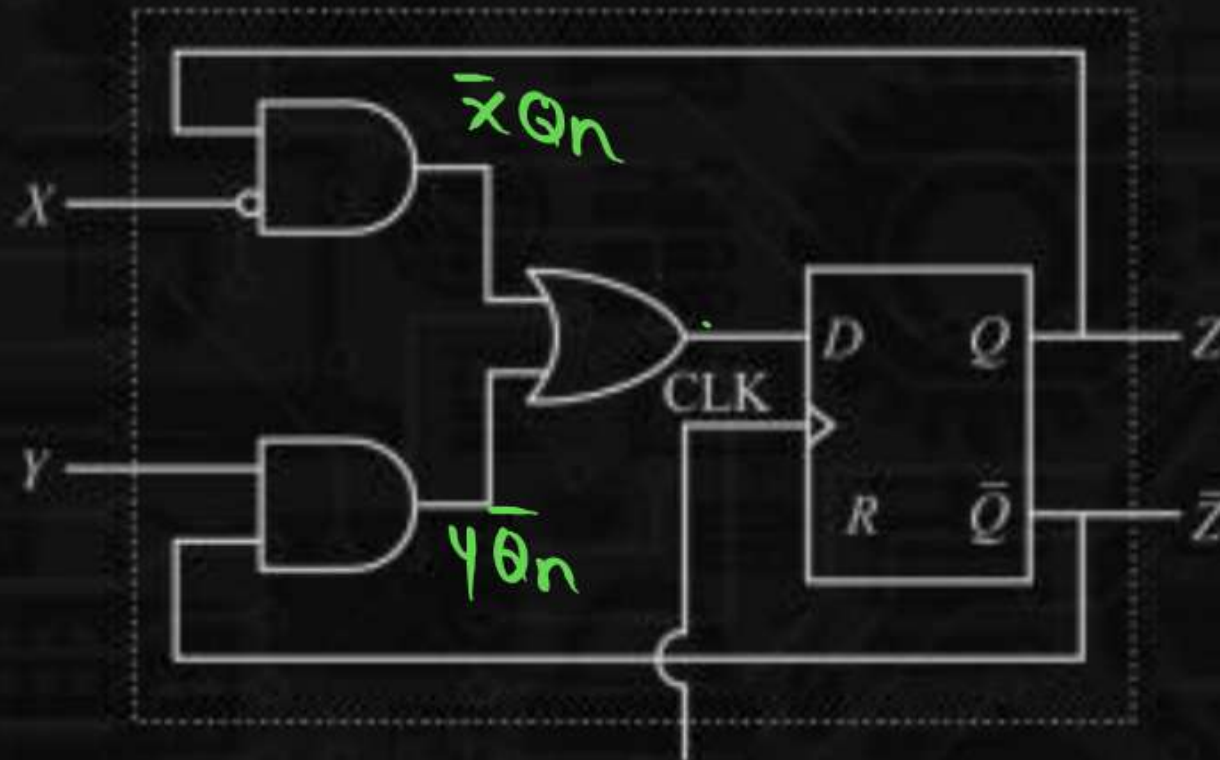

$$D = \bar{x}Q_n + y\bar{Q}_n$$

$$Q_{n+1} = D$$

$$Q_{n+1} = \bar{x}Q_n + y\bar{Q}_n$$

$$Q_{n+1} = \bar{k}Q_n + j\bar{Q}_n$$

$$X = K \quad Y = J$$

A. S-R Flip-Flop with inputs $X = R$ and $Y = S$.

B. S-R Flip-Flop with inputs $X = S$ and $Y = R$.

C. J-K Flip-Flop with inputs $X = J$ and $Y = K$.


D. J-K Flip-Flop with inputs $X = K$ and $Y = J$.

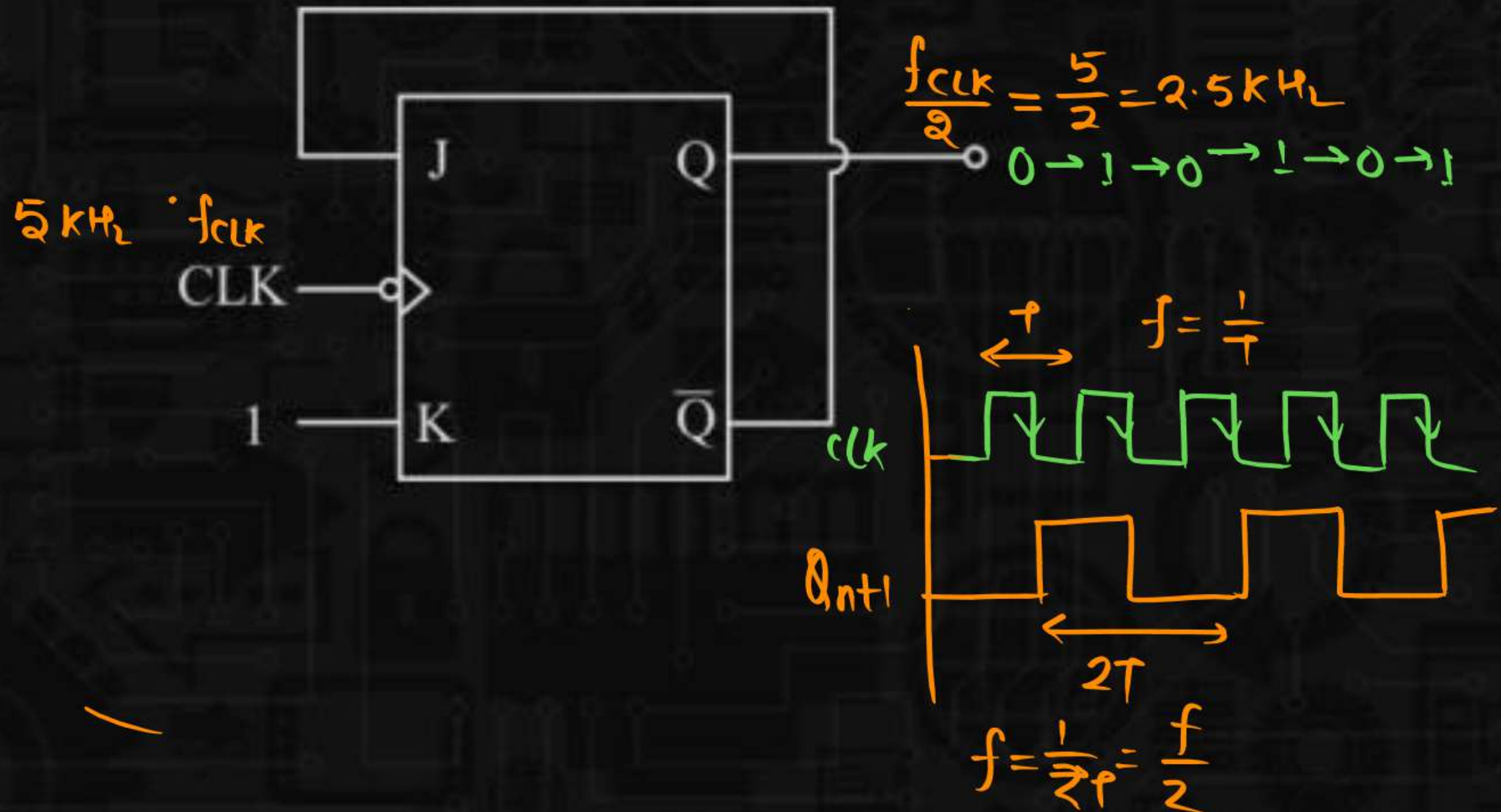Q.4

The frequency of the clock signal applied to the negative going edge triggered JK flip flop shown below is 5 kHz. What is frequency of signal available at Q ?



- ☒ A. 2.5 kHz
- ☐ B. 5 kHz
- ☐ C. 10 kHz
- ☐ D. 1.25 kHz




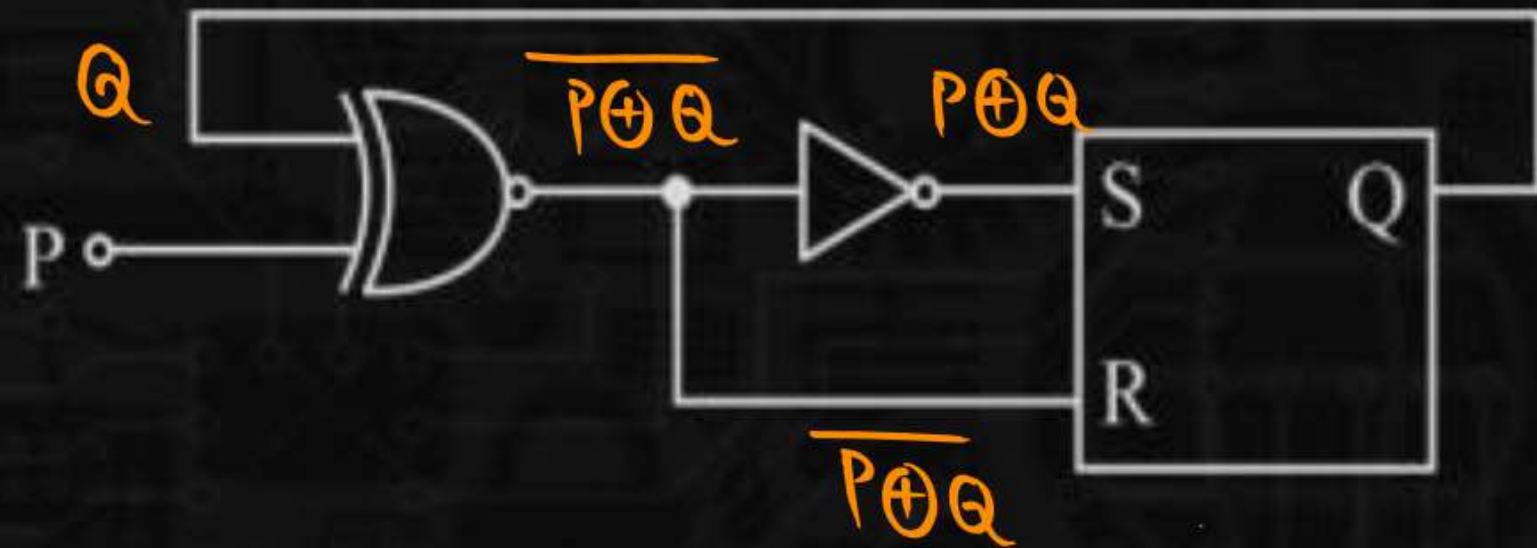Q.5

The RS flip flop is modified so as to realize a flip flop with single input P. The characteristic equation of a new flip-flop will be



- ☒ A. $Q(t+1) = P \oplus Q$
- ☐ B. $Q(t+1) = \overline{P \oplus Q}$
- ☐ C. $Q(t+1) = P + Q$
- ☐ D. $Q(t+1) = P$



$$Q_{n+1} = S + \bar{R}Q_n$$

$$= (P \oplus Q_n) + (P \oplus Q_n)Q_n$$

$$= P \oplus Q_n [1 + Q_n] = \underline{P \oplus Q_n}$$

$$S = P \oplus Q_n$$

$$R = \overline{P \oplus Q_n} = P \odot Q_n = \bar{P}\bar{Q}_n + PQ_n$$

$$\bar{R} = P \oplus Q_n$$

Q.6

The J-K FF shown below is initially cleared and then clocked for 5 pulses, the sequence at the Q output will be

A.

0 1 0 0 0 0

B.


0 1 1 0 0 1

C.

0 1 0 0 1 0

D.

0 1 0 1 0 1

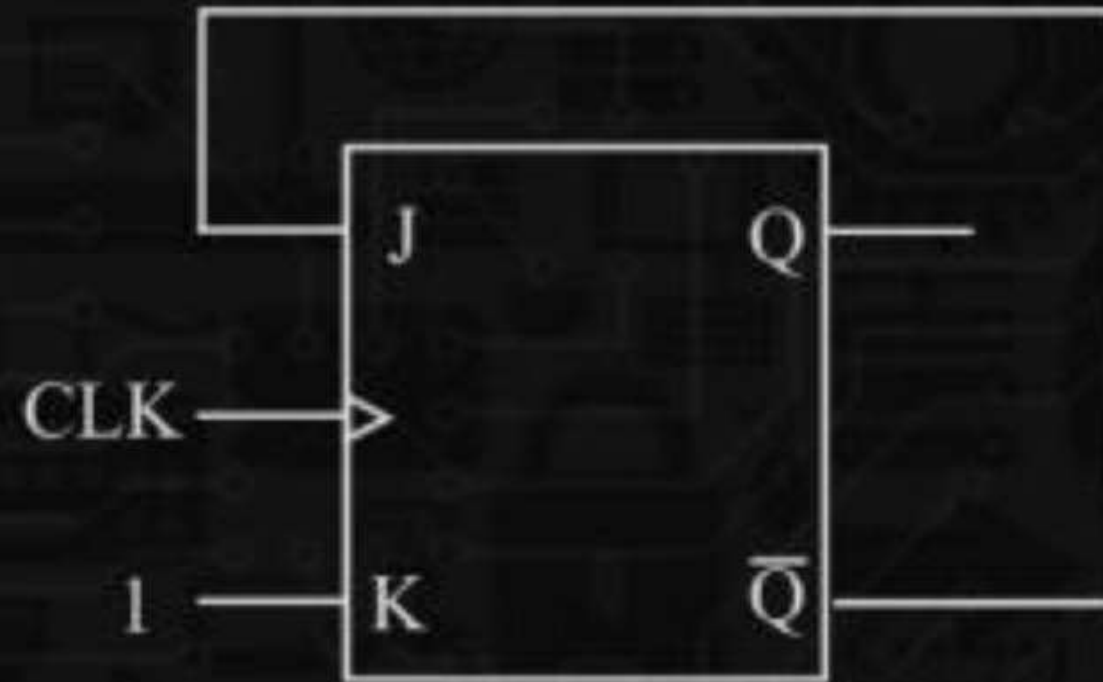

0 → 1 → 0 → 1 → 0 → 1

Q.7

For a J-K flip-flop, J input is tied to its own \bar{Q} output and its K input is connected to its own Q output. If the flip-flop is fed with a clock of frequency 1 MHz, its Q output frequency (in MHz) will be 0.5 ✓

