

DPP - 02

 
Subject : Digital Logic Chapter: Sequential Circuit



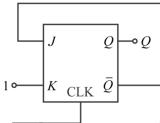


In the above J-K flip-flop, $J = \overline{Q}$ and K = 1. Assume that the flip-flop was initially cleared and then clocked for 6 pulses. What is the sequence at the Q output?

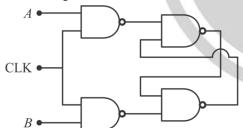- (a) 010000
- (b) 011001
- (c) 010010
- (d) 010101
- **2.** Consider the given circuit.




In this circuit, the race around

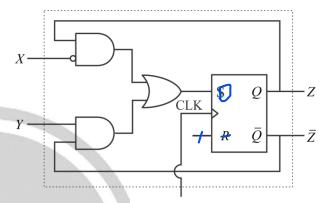
- (a) does not occur.
- (b) occurs when CLK = 0.
- (c) occurs when CLK = 1 and A = B = 1.
- (d) occurs when CLK = 1 and A = B = 0.
- **3.** A sequential circuit using *D* Flip-Flop and logic gates is shown in figure, where *X* and *Y* are the inputs and *Z* is the output. The circuit is



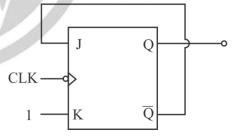- (a) S-R Flip-Flop with inputs X = R and Y = S.
- (b) S-R Flip-Flop with inputs X = S and Y = R.
- (c) J-K Flip-Flop with inputs X = J and Y = K.
- (d) J-K Flip-Flop with inputs X = K and Y = J.
- **4.** The frequency of the clock signal applied to the negative going edge triggered JK flip flop shown below is 5 kHz. What is frequency of signal available at Q?




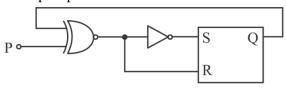- (a) 2.5 kHz
- (b) 5 kHz
- (c) 10 kHz
- (d) 1.25 kHz
- 5. The RS flip flop is modified so as to realize a flip flop with single input P. The characteristic equation of a new flip-flop will be



- (a) $Q(t+1) = P \oplus Q$
- (b) $Q(t+1) = \overline{P \oplus Q}$
- (c) Q(t+1) = P+Q
- (d) Q(t+1) = P

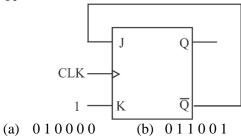6. The J-K FF shown below is initially cleared and then clocked for 5 pulses, the sequence at the *Q* output will be



- (c) 010010 (d) 010101
- 7. For a J-K flip-flop, J input is tied to its own \overline{Q} output and its K input is connected to its own Q output. If the flip-flop is fed with a clock of frequency 1 MHz, its Q output frequency (in MHz) will be_____.



Answer Key

- 1. (d)
- 2. (a)
- 3. (d)
- 4. (a)
- 5. (a)
- **6.** (**d**)
- 7. (0.5)





Any issue with DPP, please report by clicking here: $\frac{https://forms.gle/t2SzQVvQcs638c4r5}{https://smart.link/sdfez8ejd80if}$ For more questions, kindly visit the library section: Link for web: $\frac{https://smart.link/sdfez8ejd80if}{https://smart.link/sdfez8ejd80if}$

