

# CS & IT ENGINEERING

Combinational Circuit

Digital Logic

DPP – 04 Discussion notes




By- CHANDAN JHA SIR





TOPICS TO BE  
COVERED




**01** DPP Question



What are basic gates required to implement a full adder

 - A** 1 EX – OR gate, 1 AND gate
- B** 2 EX – OR gate, 1 OR gate
- C** 2 EX – OR gate, 2 AND gate, 1 OR gate
- D** 1 EX – OR gate, 2 AND gate, 2 OR gate



# Question

## NAT




How many half adders are required to implement the following expressions.

$$D = \bar{A}BC + A\bar{B}C, E = A \oplus B \oplus C$$

$$D = (\bar{A}B + A\bar{B})C \\ = (A \oplus B)C$$

$$F = \bar{A}C + AB\bar{C} + \bar{B}C$$
 
$$A \oplus B \oplus C = \bar{A}B\bar{C} + A\bar{B}\bar{C} \\ = (\bar{A} + \bar{B})C + A\bar{B}\bar{C} \\ = \bar{A}C + \bar{B}C + A\bar{B}\bar{C} \\ = F \checkmark$$






The following multiplexer circuit is equivalent to \_\_\_\_\_.

- ☒ **A** Implementation of sum equation of full adder
- ☐ **B** Implementation of carry equation of full adder
- ☐ **C** Implementation of borrow equation of full subtractor
- ☐ **D** All the above
 
$$\begin{aligned}
 Y &= a\bar{b}\bar{c} + \bar{a}\bar{b}c + \bar{a}b\bar{c} + ab\bar{c} \\
 &= \sum m(1, 2, 4, 7) = \underline{a \oplus b \oplus c} \\
 &\quad \text{sum, Niff}
 \end{aligned}$$





# Question

## MCQ




A 3 line to 8 line decoder with three inputs A, B, C and two outputs  $y_1$  and  $y_2$ , is configured as shown below. The minimized expression of outputs will be



- A**  $y_1 = \bar{A}\bar{B} + AB\bar{C}$ ;  $y_2 = \overline{A \oplus B}$
- B**  $y_1 = AB + \bar{A}\bar{B}C$ ;  $y_2 = A \oplus B$
- C**  $y_1 = \bar{A}B + A\bar{C}$ ;  $y_2 = AB + AC$
- D**  $y_1 = A\bar{B} + \bar{A}C$ ;  $y_2 = \bar{A}B + \bar{B}C$

A \ BC				
	00	01	11	10
0	1	1		
1				1

$= \bar{A}\bar{B} + AB\bar{C}$

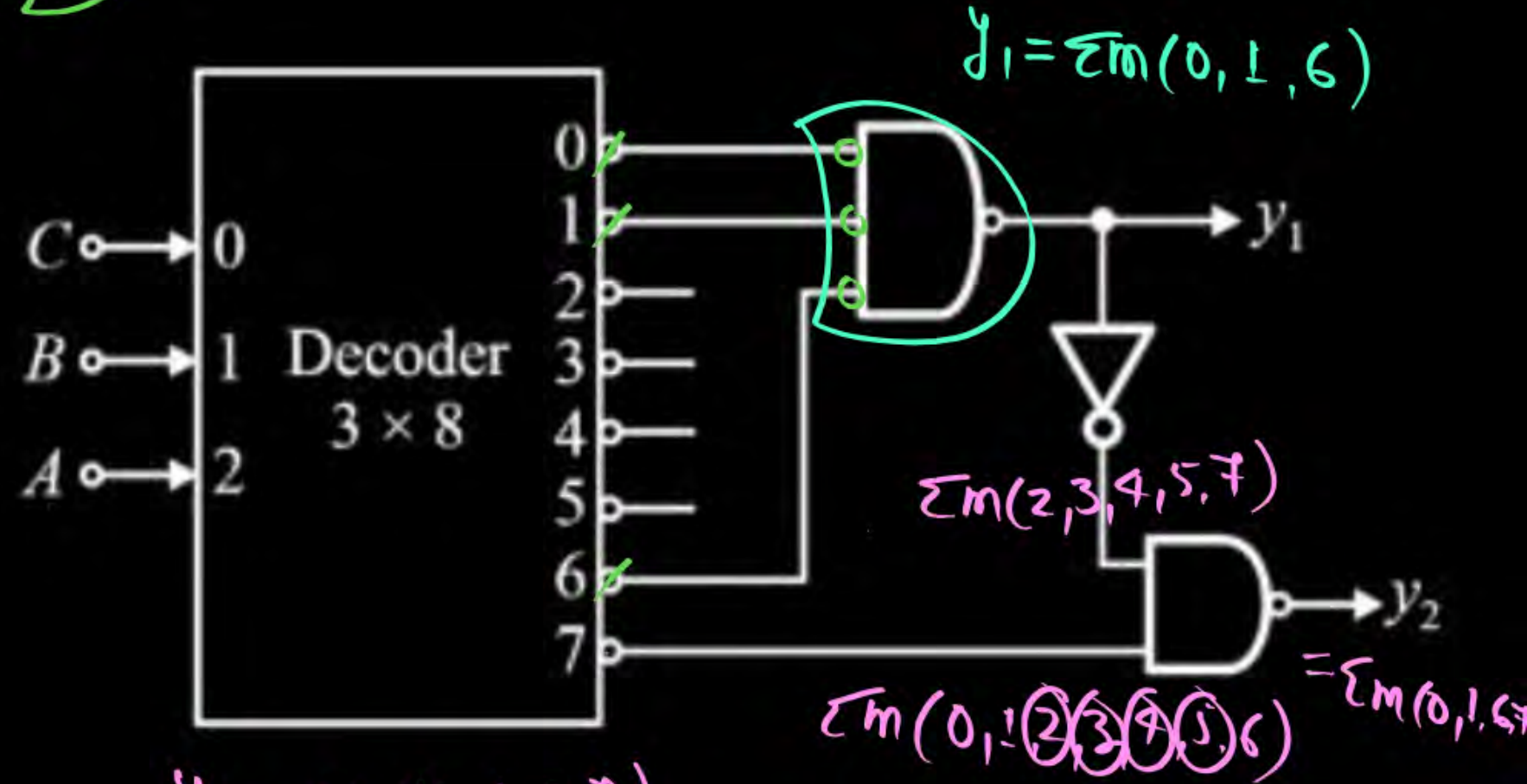

$$y_2 = \Sigma m(0, 1, 6, 7)$$

$$= \bar{A}\bar{B} + AB = A \odot B = \overline{A \oplus B}$$




## Question
 
## MCQ



A demultiplexer of size  $1 \times 8$  with active low outputs, is programmed as shown below. The circuit has three inputs  $x, y, z$  and generates two outputs  $y_1, y_2$ .




What is this circuit

- ☐ A Half subtractor
- ☐ B Full subtractor
- ☐ C Half adder
- ☒ D Full adder



The logic diagram of a  $3 \times 8$  decoder with active low outputs is shown below. What is state of outputs  $Q_7, \dots, Q_0$  for the set of inputs  $E_3 = E_1 = 1$ ,  $E_2 = 0$ ,  $A_2 = A_1 = 1$  and  $A_0 = 0$ ?

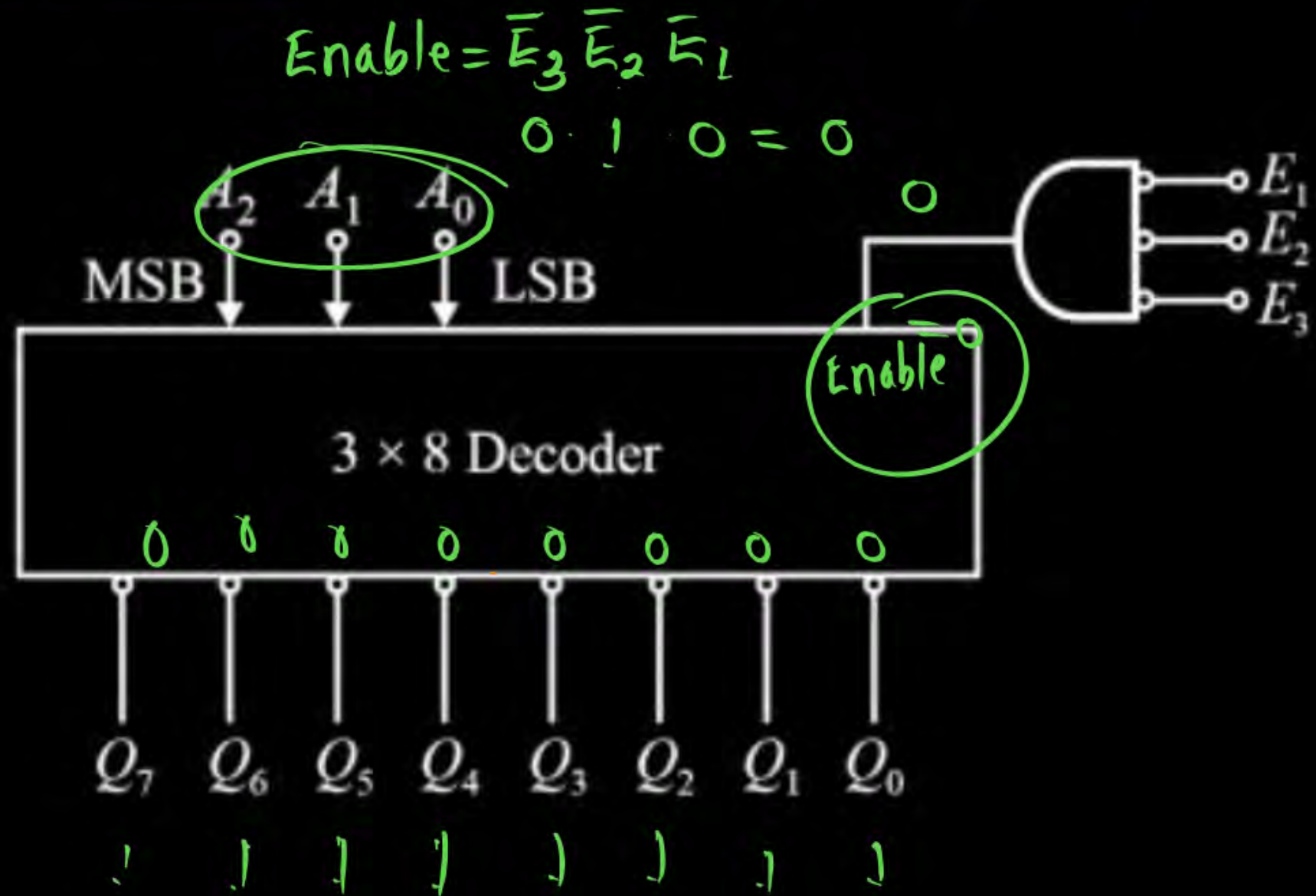- A** 1111 1111
- B** 1011 1111
- C** 1111 0111
- D** 0000 0000





A 3 line to 8 line decoder with active low outputs, is used to realize Boolean function involving three variables  $x$ ,  $y$  and  $z$  ( $x$  is MSB and  $z$  is LSB) as shown below.

The minimized Boolean function  $f(x, y, z)$  in POS format, will be

$$f = \sum m(1, 3, 5, 6)$$

**A**  $(\bar{x} + \bar{y} + \bar{z})(x + y + z)(x + \bar{y} + \bar{z})(\bar{x} + y + \bar{z})$


**B**  $(\bar{x} + \bar{y} + z)(\bar{x} + y + z)(x + \bar{y} + z)(x + y + \bar{z})$

**C**  $(x + z)(y + z)(\bar{x} + \bar{y} + \bar{z})$

**D**  $(\bar{x} + \bar{z})(\bar{y} + \bar{z})(x + y + z)$

$$(x+z)(y+z)(\bar{x}+\bar{y}+\bar{z})$$

$x \backslash yz$	00	01	11	10
$x$	0	1	1	0
$\bar{x}$	0	1	0	1

 




Two  $2 \times 4$  decoders one with active low outputs and another with active high output are interconnected as shown below. The output function  $f_2(x_3, x_2, x_1)$  will be

**A**  $f_2 = (x_1 \oplus x_2) \odot x_3$

**B**  $f_2 = (x_1 \odot x_2) \odot x_3$

**C**  $f_2 = (x_1 \oplus x_2) \oplus x_3$

 **D**  $f_2 = (x_1 \oplus x_2) \oplus x_3$



$$f_2 = \bar{x}_3 \bar{f}_1 + x_3 f_1$$

$$= x_3 \odot f_1 = x_3 \odot (x_2 \oplus x_1)$$



Three half adders  $HA_1$ ,  $HA_2$  and  $HA_3$  are inter-coupled as shown below. The four output functions  $y_1$ ,  $y_2$ ,  $y_3$  and  $y_4$  are expressed in terms of inputs  $a$ ,  $b$  and  $c$ . Which one of the following output expressions, is correct?


**A**  $y_1 = (a \oplus b)c$  ✗

**B**  $y_2 = (a \oplus b) \oplus c$  ✗

**C**  $y_3 = ab \oplus c$  ✓

**D**  $y_4 = a(b \oplus c)$

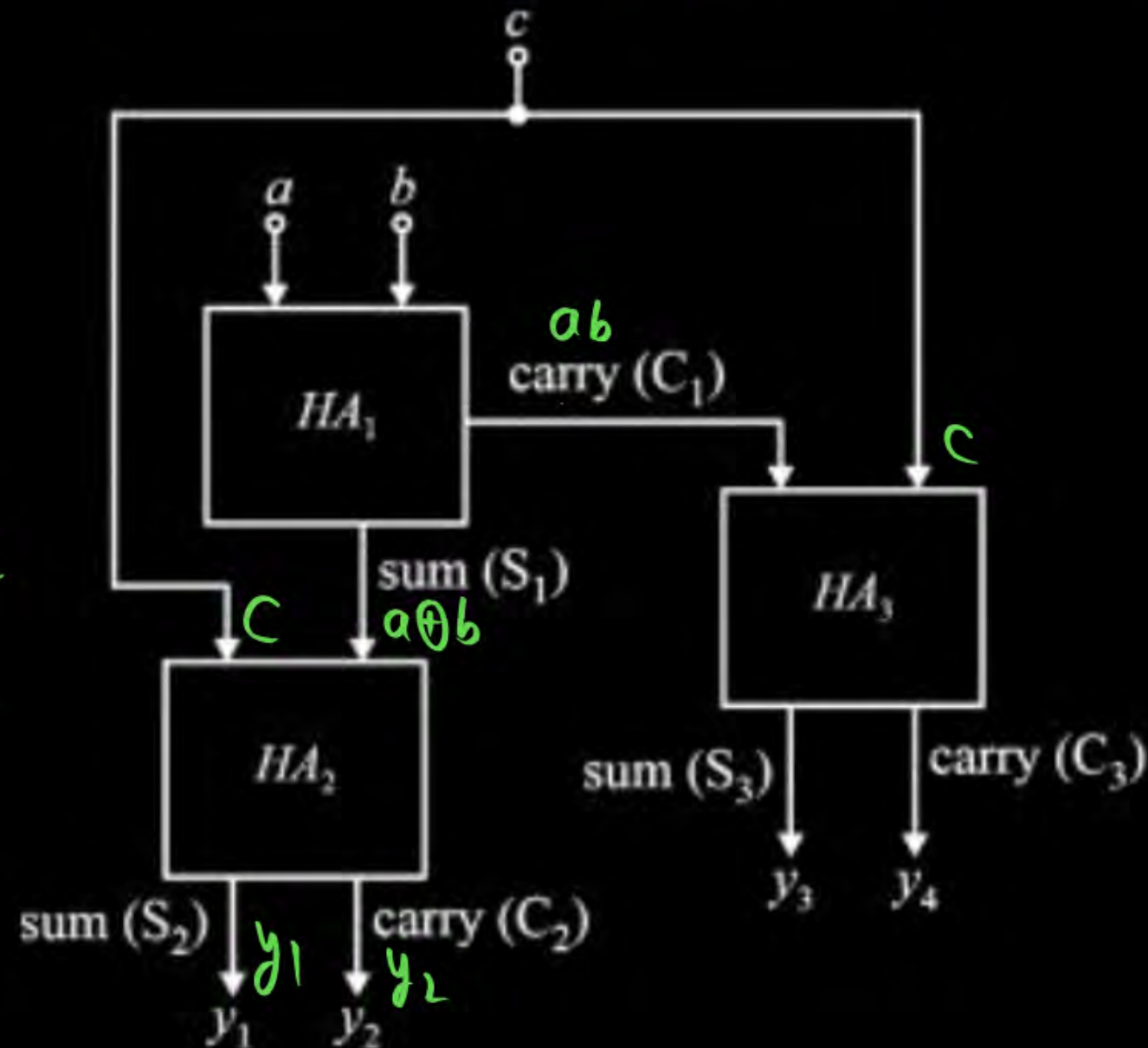$y_1 = a \oplus b \oplus c$   
 $y_2 = (a \oplus b)c$   
 $y_3 = ab \oplus c$   
 $y_4 = abc$






Determine the outputs for the circuit shown below.

**A**  $\Sigma' = 1, C'_{out} = 1$

**B**  $\Sigma' = 0, C'_{out} = 0$

**C**  $\Sigma' = 0, C'_{out} = 1$

**D**  $\Sigma' = 1, C'_{out} = 0$

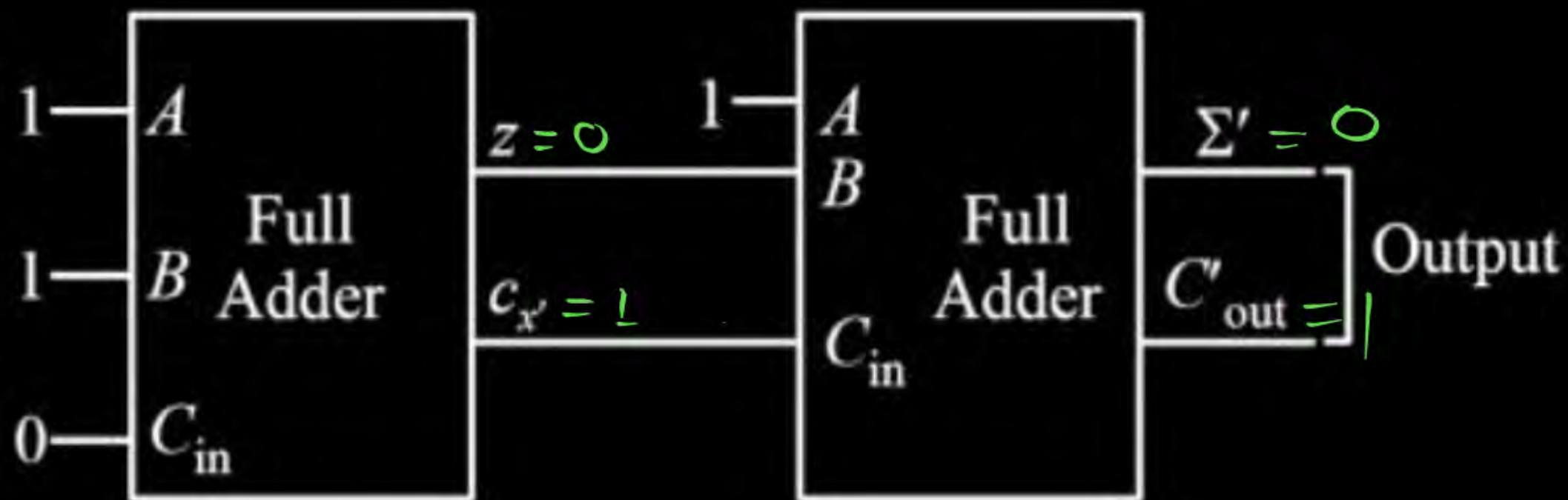

$$1+0+1$$

How many half adders, will be required to add two k bit numbers?

**A**  $2k + 1$


**B**  $2k - 1$

**C**  $2k$

**D**  $2(k + 1)$

4 bit

7 H.A + 1 OR

 

k bits

$(2k-1) \text{ H.A} + (k-1) \text{ OR}$



Eight 1-bit full adders are cascaded. Each 1-bit full adder generates carry out bit in 10 ns and sum bit in 30 ns. The number of addition performed per second, will be 1  $\times 10^7$

$$n = 8$$

$$T = (n-1)T_{\text{carry}} + \text{Max}\{T_{\text{sum}}, T_{\text{carry}}\}$$

$$= \{7 \times 10 + 30\} \text{ ns}$$

$$T = \underline{100 \text{ ns}}$$

$$\frac{1}{T} = \frac{1}{100 \times 10^{-9}} = \frac{100 \times 10^7}{100} = \underline{1 \times 10^7}$$

Thank you

**GW**  
*Soldiers !*

