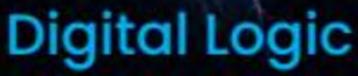






ENGINEERING






DPP - 03 Discussion Notes

Combinational Circuit






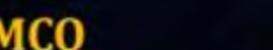






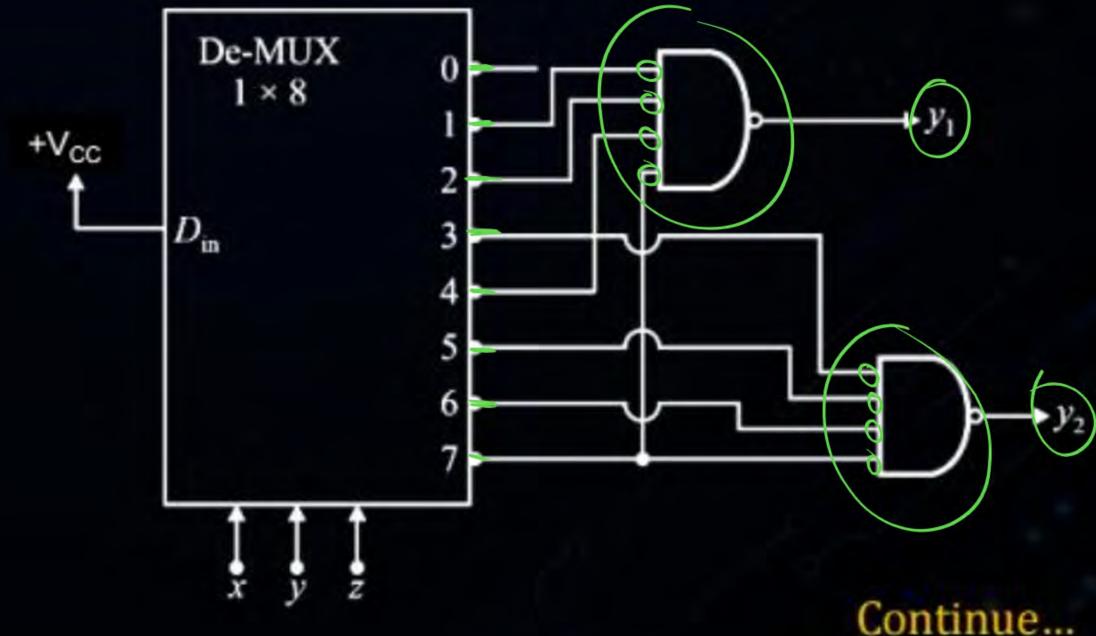
A demultiplexer of size 1×8 with active low outputs, is programmed as shown below. The circuit has three inputs x, y, z and generates two outputs y_1, y_2 .



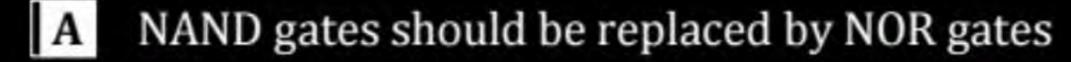If de-multiplexer has active high output instead of active low outputs, then in order that outputs do not change



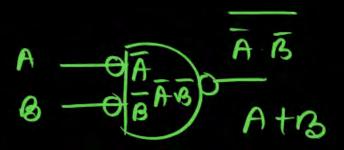- B NAND gates should be replaced by OR gates
- C NAND gates should be replaced by AND gates
- D The inputs x, y, z should be inverted










For what values of A, B, C the output (Y) will be 0

$$A \times A = 1, B = 0, C = 0$$

$$B = 0, B = 1, C = 1$$

$$A = 1, B = 1, C = 0$$

D
$$A = 1, B = 1, C = 1$$

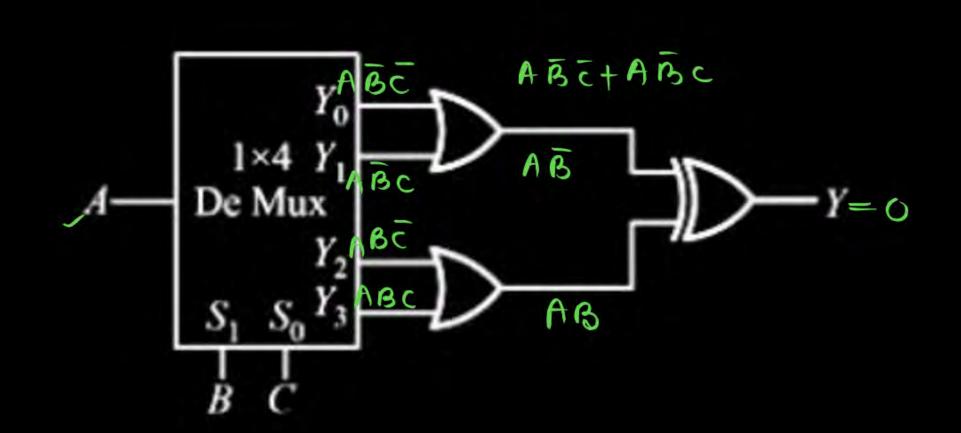

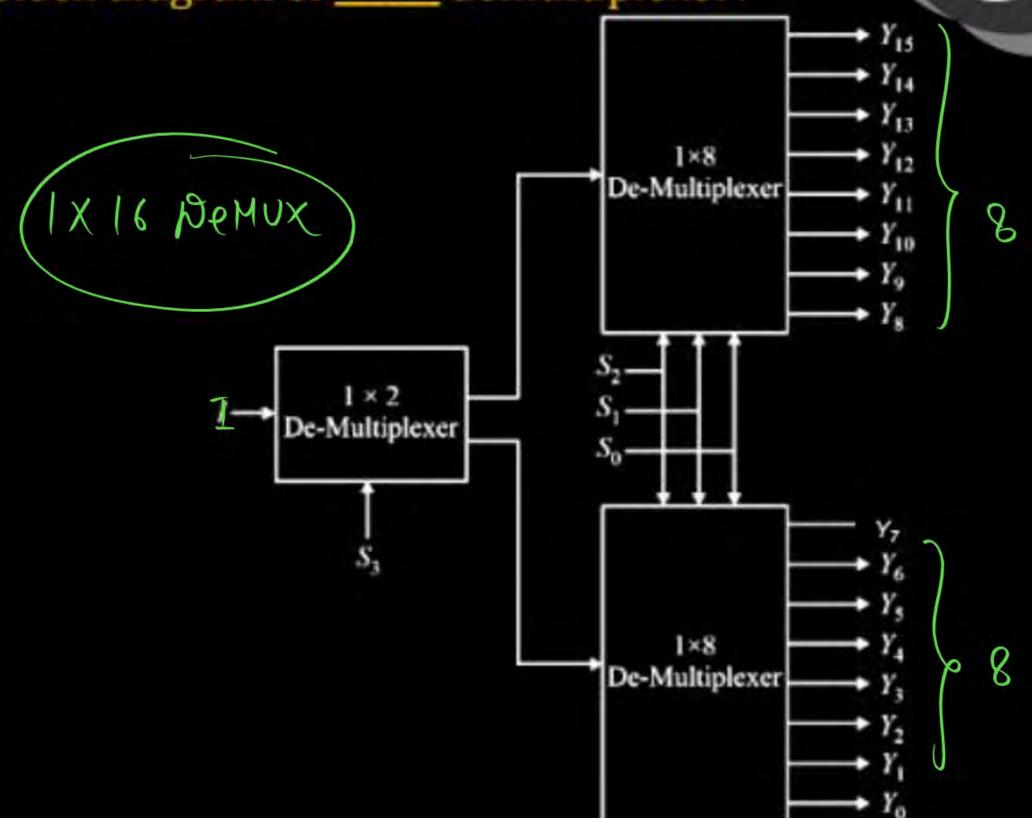
Question MCQ

The figure shown below is a block diagram of _____ demultiplexer?





- B 1 to 8
- C 1 to 16
- D None of the above




MCQ







Identify the circuit shown below?

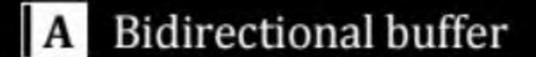

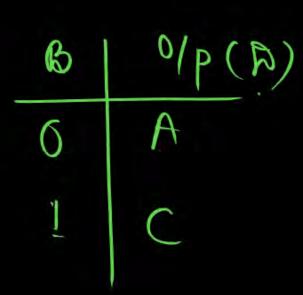- B De-multiplexer
- C Multiplexer
- D Encoder



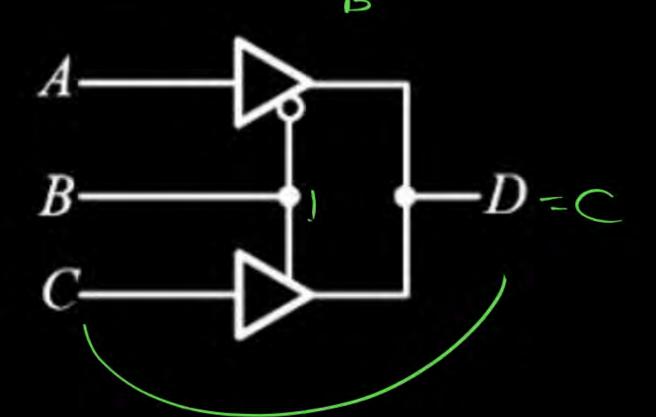

B

A





How many inputs will a decimal to BCD encoder have?

Question MCQ





Which one of the following de multiplexer requires only five select lines?

B
$$1 \times 4$$
 De Mux

$$D = 1 \times 32 De Mux$$

$$32 = 2^{5}$$

$$n = |0 \cdot 2^n$$

Question NAT





What is the minimum number of 1×4 De Mux required to implement 1×2^{10} De Mux. 341

$$1 \times 4 \text{ DEMUX} = \frac{1024}{4} + \frac{256}{4} + \frac{64}{4} + \frac{16}{4} + \frac{4}{4} + \frac{4}{4} + \frac{1}{4} +$$

$$320+21$$
 $=(341)$
Ass





To implement a 1: 128 De-Mux we require M number of 1:8 De-mux

and N numbers of 1:2 De-mux.


Then which of the following is correct?

$$A/(M-N)/2 = 9$$

$$B/M + N = M$$

$$C/M/N = M$$

$$D (M + N)/2$$

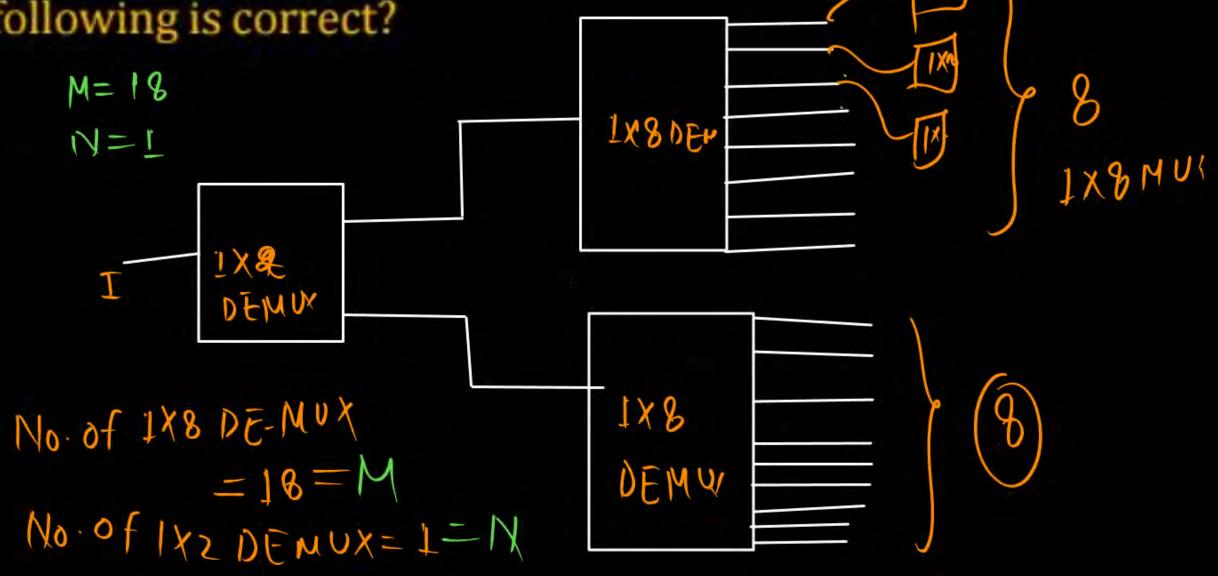

Question MCQ






Consider a circuit as shown below: Output y is?



$$\mathbf{B} \quad \overline{A \cdot B}$$

$$C / A \oplus B$$

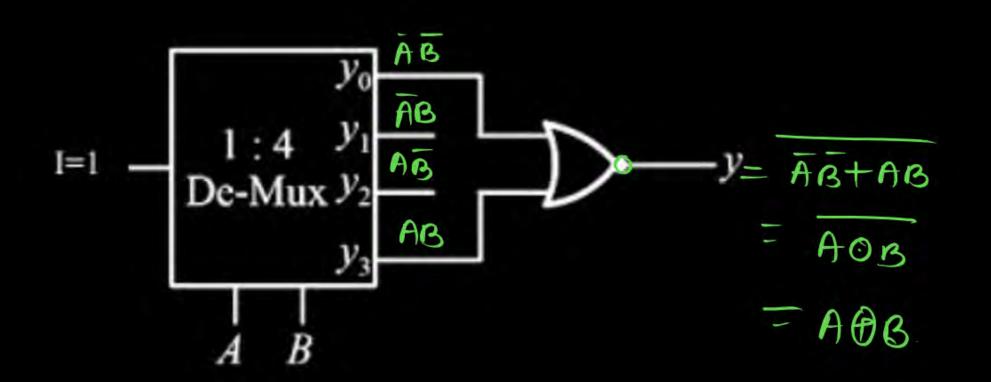


MCQ





Consider an combinational circuit as shown below. For any sequence of A,B which of the output pins $(y_0 \text{ to } y_3)$ can be active

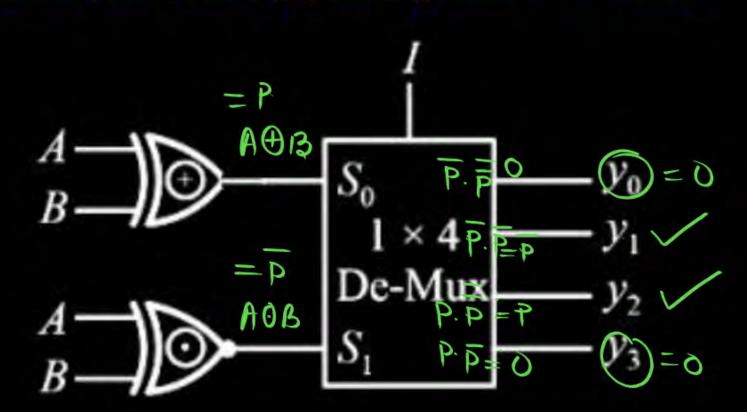- A y_0 and y_3 only
- y_1 and y_2 only
- C y_1 only
- D all pins can be active





Thank you

Seldiers!

