CS & IT ENGINEERING

Digital Logic


Logic Gate




Discussion Notes

By- CHANDAN SIR



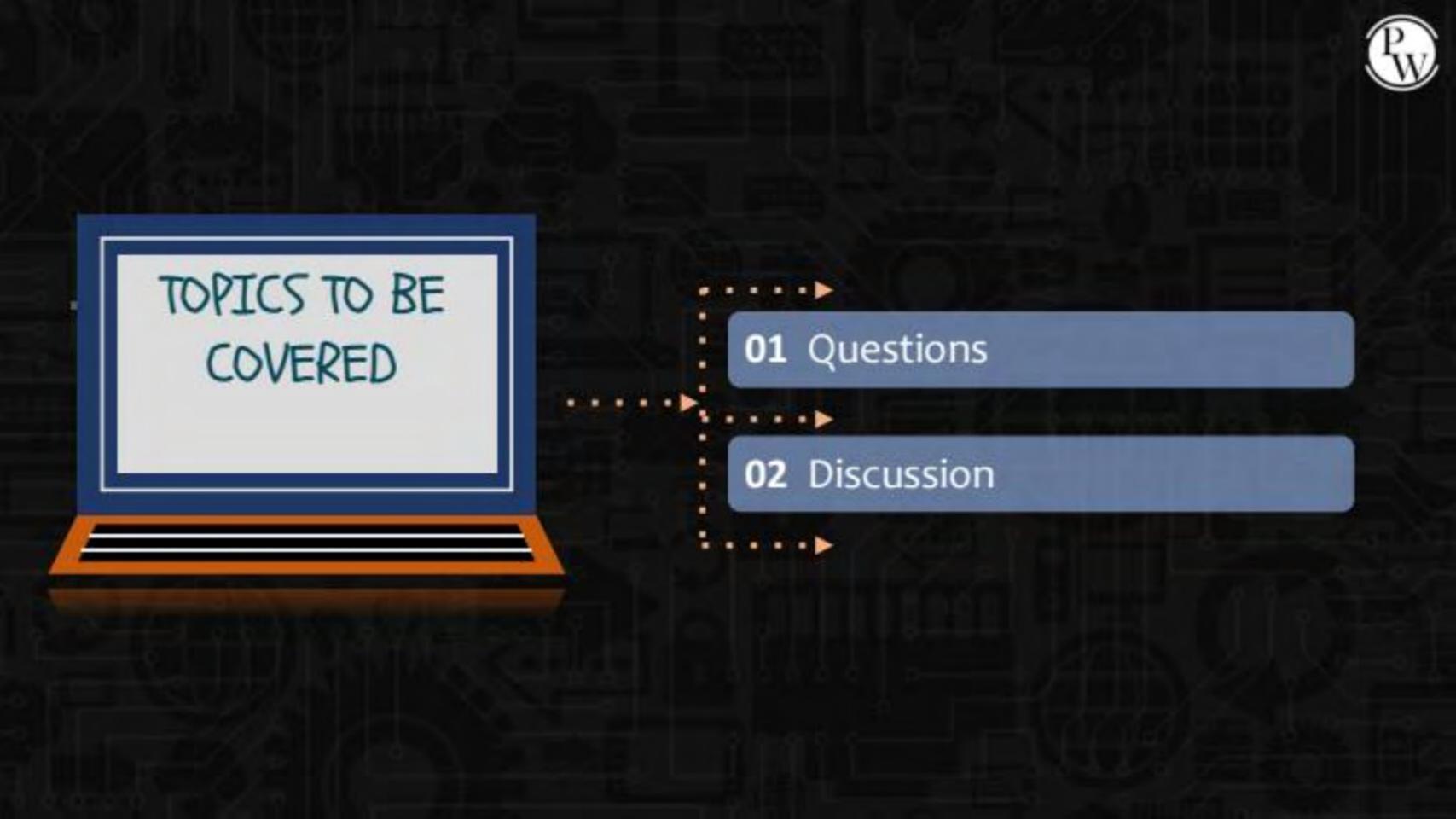


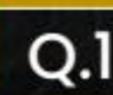

The input wave form is given



$$A \cdot 1 = A$$

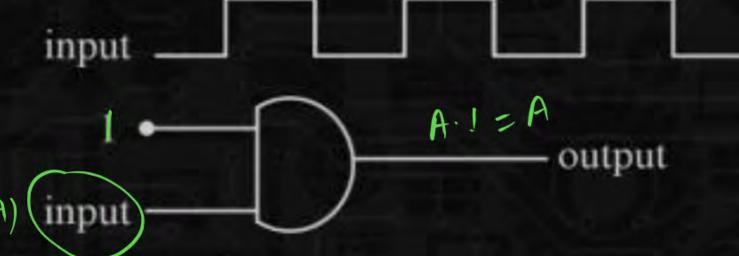


Draw output wave form









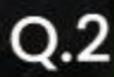


When A = 1 then the value of Y equal





0

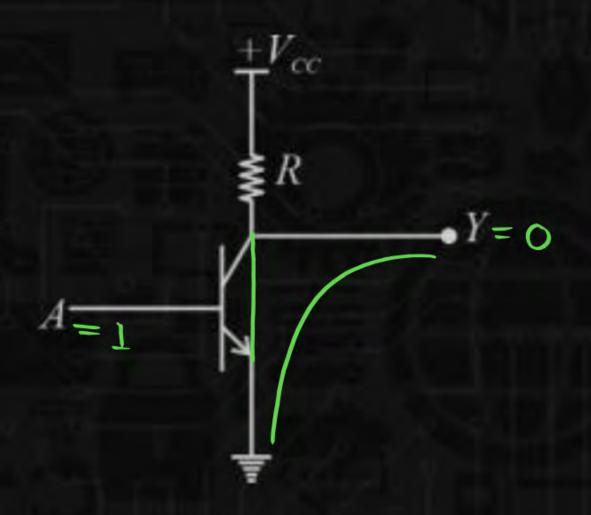
- B. 1
- c. V_{cc}
- D. none of the above






input


input=0 OFF input=1 ON

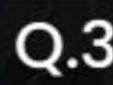



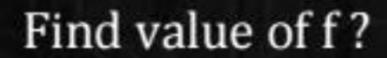

- A. 1
- B. 0
- C. A

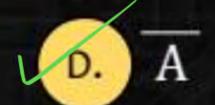





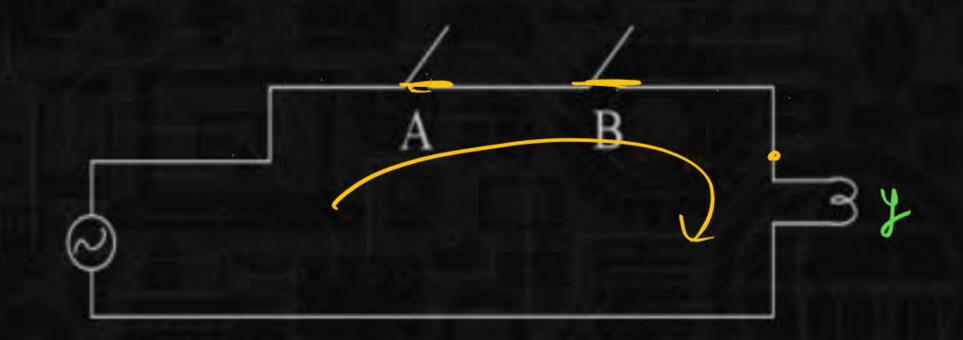
Q.4

Bulb will glow when A and B are respectively.










A	B	y
0	0	0
0	1	0
1	0	0
1	1	1]

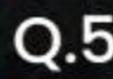

Find expression of F





$$\overline{A}BC + D\overline{E}$$





 $\bar{A}BCD\bar{E}$

$$(\bar{A} + BC)D\bar{E}$$



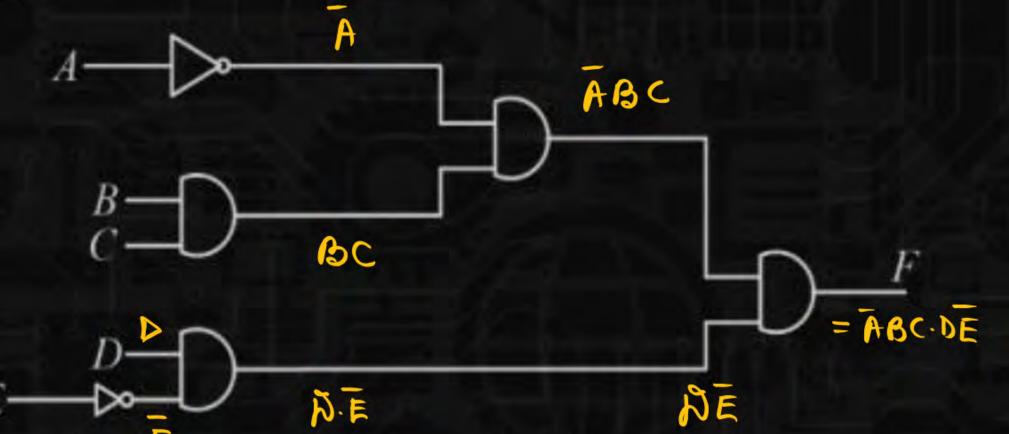
$$\overline{A}BC\left(D+\overline{E}\right)$$



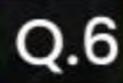

The inverter is _____ gate



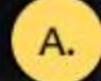

AND

- B. OR
- NOT
 - D. none of the above

Inverter, Negation, Not GIATE

Complement Logic

Q.7

Find expression of f?







AB

В.

A + B

D. \overline{AB}

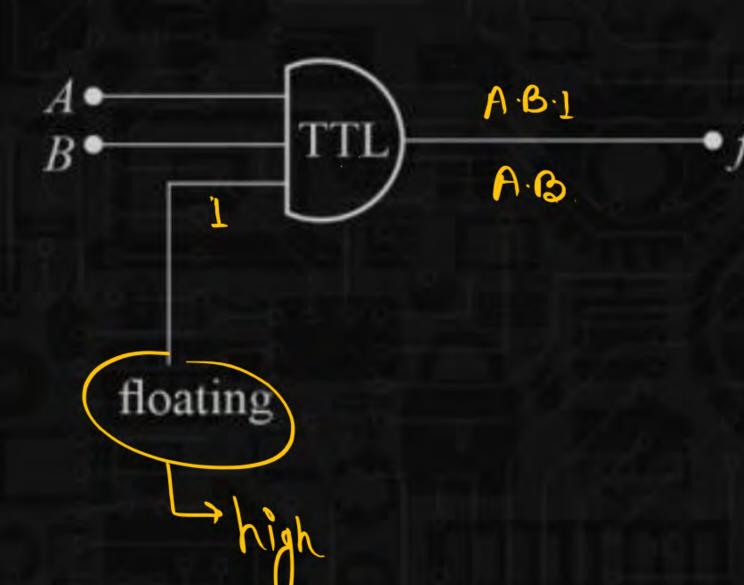

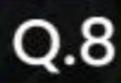


Find expression of f?






0

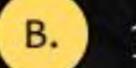


1



D.

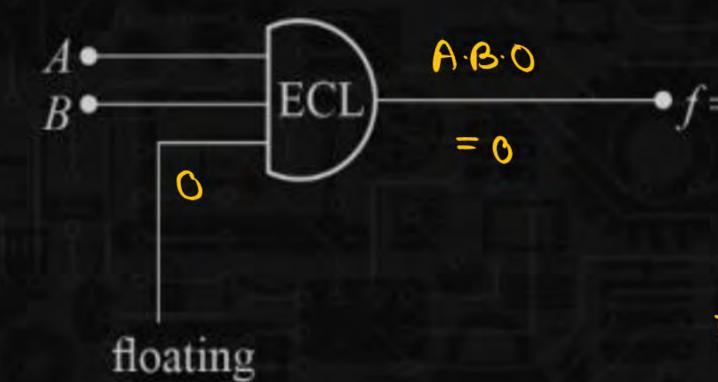

E(L > Emitter coupled Logic

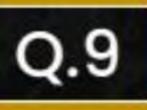

Find output frequency, if the propagation delay of NOT gate is 2 n sec.



- A. 125 MHz
- B. 500 MHz
- 250 MHz
- D. none of the above



$$f = \frac{1}{211 \times CPd} = \frac{1}{2 \times 1 \times 2 \times 10^9} \frac{1}{\text{Sec}} (H_2)$$

$$= \frac{10^9}{4} H_2$$



